# 基于Verilog和FPGA的多功能秒表设计

刘书畅 518021910789

# 实验目的

- 1. 初步掌握利用Verilog硬件描述语言进行逻辑功能设计的原理和方法
- 2. 理解和掌握运用大规模可编程逻辑器件进行逻辑设计的原理和方法
- 3. 理解硬件实现方法中的并行性, 联系软件实现方法中的并发性
- 4. 理解硬件和软件是相辅相成、并在设计和应用方法上的优势互补的特点
- 5. 本实验学习积累的Verilog硬件描述语言和对FPGA/CPLD的编程操作,是进行后续《计算机组成原理》部分课程实验,设计实现计算机逻辑的基础


# 设计思路

由于这是本人第一次接触相关实验,所以采取先减后繁,逐步迭代的设计思路。先实现简单的控制数码管显示,并亮起相应数字,再实现时间计数功能。当完成基础功能后逐步加上按键功能,LED灯功能。最后增加按键消抖。

#### 1. 数码管显示

一个数字由七根数码管组成,所以需要7个bit控制。使用case语句,进行不同数字到数码管亮暗的转换。1表示暗,0表示亮。

数码管的不同管的亮暗由不同bit控制

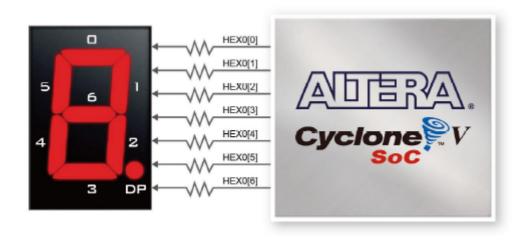

# 2. 时间计数功能设计

因为DE1-SOC板上的时钟为50MHz, 所以需要500000次20ns之后, 才是10ms。

而要求设计的秒表需要精确到10ms,所以我们使用变量 counter\_50m 进行计数,每次时钟上升沿将计数器加一,当计数器的值为500000时,说明时间累积10ms,相应增加 msecond\_display\_low 的值。

为了数码管同时改变值,和为之后的暂停显示功能做准备,我们区分计数寄存器和显示寄存器, XXX\_counter\_high/low用于计数,XXX\_display\_high/low用于显示,若需要显示当前时间,则把 计数值赋值给显示值。

不同时间位之间的进制不同。 msecond\_counter\_low 满10, msecond\_counter\_high 加一; msecond\_counter\_high 满10, second\_counter\_low 加一; second\_counter\_low 满10, second\_counter\_high 满6, minute\_counter\_low 加一; minute\_counter\_low 满10, minute\_counter\_high 加一。

### 3. 按键功能设计

按照需求,我们需要设计三个按键,分别为"计时复位"、"计数/暂停"、"显示暂停/显示继续"。我们采用 KEYO 控制计时复位,用 KEY1 控制计数/暂停,用 KEY2 控制显示暂停/显示继续。

按键按下信号为0。

使用 reset\_time 表示是否需要复位,若为1则将 xxx\_counter\_high/low 和计数器 counter\_50M 均置为0,并赋值给 xxx\_display\_high/low。

使用 start 表示是否开始计时。只有 start 为1时才改变 xxx\_counter\_high/low 的值。


使用 display 表示是否开始显示。只有 display 的值为1时,才将 xxx\_counter\_high/low 赋值给 xxx\_display\_high/low。

#### 4. LED灯设计

LEDRO 表示"计时复位"按键是否按下,LEDR1表示"计数/暂停"按键是否按下,LEDR2表示"显示暂停/显示继续"按键是否按下。按键按下LED灯为暗。
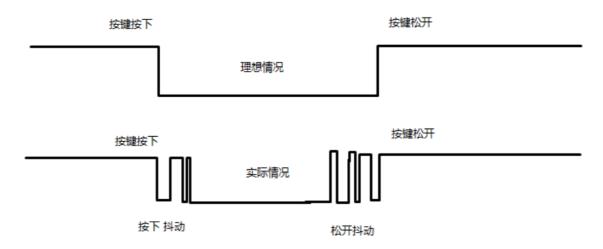
# 5. 按键消抖

按键按下的理想状态波形应该如图所示,但由于人手的不精确以及材料的形变回弹等等原因,往往不能达到理想情况。



按键消抖的总体思路为忽略抖动时的信号变化。

此处我进行按键消抖的思路为,当按键按下时开始计数,当持续有 8'b11111111 次,按键信号为按下时,表示按键真的按下,修改相应 reset\_time, start, display 的值。当按键松开时开始计数,当持续有 8'b11111111 次,按键信号为松开时,表示按键真的松开。

由于 reset 操作较开始和显示简单,所以松开按键不做计数。

# 代码说明

一下对关键代码进行说明

### 1. 时间计数

每次时钟上升沿增加计数器 counter\_50m的值, 当 if(counter\_50m == 500000) 时, 说明累积 10ms, 逐级判断进位。

```
if(start)
   begin
   counter_50M = counter_50M + 1;
        if(counter_50M == 500000)
        begin
        counter_50M = 0;
        msecond_counter_low = msecond_counter_low + 1;
            if(msecond_counter_low == 10)
            begin
            msecond_counter_high = msecond_counter_high + 1;
            msecond_counter_low = 0;
                if(msecond_counter_high == 10)
                begin
                msecond_counter_high = 0;
                second_counter_low = second_counter_low +1;
                    if(second_counter_low == 10)
                    begin
                    second_counter_low = 0;
                    second_counter_high = second_counter_high +1;
                        if(second_counter_high == 6)
                        begin
                        minute_counter_low = minute_counter_low +1;
                        second_counter_high =0;
                            if(minute_counter_low == 10)
                            begin
                            minute_counter_low = 0;
                            minute_counter_high = minute_counter_high +1;
                                if(minute_counter_high ==6)
                                minute_counter_high = 0;
                            end
                        end
                    end
                end
            end
        end
```

# 2. 按键消抖

此处以"计数/暂停"的按键消抖为例。

当按键完成按下并松开这一动作时,才视为一次成功按键操作,转换 start 状态。

start\_time 变量用于按键消抖状态转换,start\_time 值为1时进行按下计数,为0时进行松开计数。

```
always @(posedge CLOCK_50)
begin
if (start_time && !key_start_pause)
 begin
   counter_start = counter_start + 1;
  if (counter_start == 8'b111111111)
   begin
     counter_start = 0;
     start_time = ~start_time;
   end
 end else if (!start_time && key_start_pause)
    begin
     counter_start = counter_start + 1;
     if (counter_start == 8'b11111111)
     begin
      counter_start = 0;
       start_time = ~start_time;
       start = !start;
     end
   end else
   begin
     counter_start = 0;
   end
end
```

# 3. 时序设置

```
create_clock -name "CLOCK_50" -period 20.000ns [get_ports {CLOCK_50}]
derive_clock_uncertainty
```

# 4. 引脚分配

完成代码编写后需要将对应原件映射到对应的引脚上,根据《DE1-SoC User Manual》

#### LED灯的映射如下:

Table 3-8 Pin Assignment of LEDs

Signal Name	FPGA Pin No.	Description	I/O Standard
LEDR[0]	PIN_V16	LED [0]	3.3V
LEDR[1]	PIN_W16	LED [1]	3.3V
LEDR[2]	PIN_V17	LED [2]	3.3V
LEDR[3]	PIN_V18	LED [3]	3.3V
LEDR[4]	PIN_W17	LED [4]	3.3V
LEDR[5]	PIN_W19	LED [5]	3.3V
LEDR[6]	PIN_Y19	LED [6]	3.3V
LEDR[7]	PIN_W20	LED [7]	3.3V
LEDR[8]	PIN_W21	LED [8]	3.3V
LEDR[9]	PIN_Y21	LED [9]	3.3V

#### 数码管的映射如下:

Table 3-9 Pin Assignment of 7-segment Displays

Signal Name	FPGA Pin No.	Description	I/O Standard
HEX0[0]	PIN_AE26	Seven Segment Digit 0[0]	3.3V
HEX0[1]	PIN_AE27	Seven Segment Digit 0[1]	3.3V
HEX0[2]	PIN_AE28	Seven Segment Digit 0[2]	3.3V
HEX0[3]	PIN_AG27	Seven Segment Digit 0[3]	3.3V
HEX0[4]	PIN_AF28	Seven Segment Digit 0[4]	3.3V
HEX0[5]	PIN_AG28	Seven Segment Digit 0[5]	3.3V
HEX0[6]	PIN_AH28	Seven Segment Digit 0[6]	3.3V
HEX1[0]	PIN_AJ29	Seven Segment Digit 1[0]	3.3V
HEX1[1]	PIN_AH29	Seven Segment Digit 1[1]	3.3V
HEX1[2]	PIN_AH30	Seven Segment Digit 1[2]	3.3V
HEX1[3]	PIN_AG30	Seven Segment Digit 1[3]	3.3V
HEX1[4]	PIN_AF29	Seven Segment Digit 1[4]	3.3V
HEX1[5]	PIN_AF30	Seven Segment Digit 1[5]	3.3V
HEX1[6]	PIN_AD27	Seven Segment Digit 1[6]	3.3V
HEX2[0]	PIN_AB23	Seven Segment Digit 2[0]	3.3V
HEX2[1]	PIN_AE29	Seven Segment Digit 2[1]	3.3V
HEX2[2]	PIN_AD29	Seven Segment Digit 2[2]	3.3V
HEX2[3]	PIN_AC28	Seven Segment Digit 2[3]	3.3V
HEX2[4]	PIN_AD30	Seven Segment Digit 2[4]	3.3V
HEX2[5]	PIN_AC29	Seven Segment Digit 2[5]	3.3V
HEX2[6]	PIN_AC30	Seven Segment Digit 2[6]	3.3V
HEX3[0]	PIN AD26	Seven Segment Digit 3[0]	3.3V
HEX3[1]	PIN_AC27	Seven Segment Digit 3[1]	3.3V
HEX3[2]	PIN AD25	Seven Segment Digit 3[2]	3.3V
HEX3[3]	PIN AC25	Seven Segment Digit 3[3]	3.3V
HEX3[4]	PIN AB28	Seven Segment Digit 3[4]	3.3V
HEX3[5]	PIN AB25	Seven Segment Digit 3[5]	3.3V
HEX3[6]	PIN AB22	Seven Segment Digit 3[6]	3.3V
HEX4[0]	PIN AA24	Seven Segment Digit 4[0]	3.3V
HEX4[1]	PIN_Y23	Seven Segment Digit 4[1]	3.3V
HEX4[2]	PIN Y24	Seven Segment Digit 4[2]	3.3V
HEX4[3]	PIN W22	Seven Segment Digit 4[3]	3.3V
HEX4[4]	PIN_W24	Seven Segment Digit 4[4]	3.3V
HEX4[5]	PIN V23	Seven Segment Digit 4[5]	3.3V
HEX4[6]	PIN_W25	Seven Segment Digit 4[6]	3.3V
HEX5[0]	PIN V25	Seven Segment Digit 5[0]	3.3V
HEX5[1]	PIN_AA28	Seven Segment Digit 5[1]	3.3V
HEX5[2]	PIN_Y27	Seven Segment Digit 5[2]	3.3V
HEX5[3]	PIN AB27	Seven Segment Digit 5[3]	3.3V
HEX5[4]	PIN_AB26	Seven Segment Digit 5[4]	3.3V
			3.3V
HEX5[5]	PIN_AA26	Seven Segment Digit 5[5]	3.34

按键的映射如下:

Table 3-7 Pin Assignment of Push-buttons

Signal Name	FPGA Pin No.	Description	I/O Standard	
KEY[0]	PIN_AA14	Push-button[0]	3.3V	
KEY[1]	PIN_AA15	Push-button[1]	3.3V	
KEY[2]	PIN_W15	Push-button[2]	3.3V	
KEY[3]	PIN_Y16	Push-button[3]	3.3V	

#### 参考文献:

- 1. 《软件学院《数字系统设计》课程实验指导书 (2018级) 交大》
- 2. 《DE1-SoC User Manual》
- 3. 《My\_First\_Fpga》